

**8 (a)** Complete the truth tables for the following logic gates.

AND Gate		
Input X	Input Y	Output Q
0	0	
0	1	
1	0	
1	1	

XOR Gate		
Input X	Input Y	Output Q
0	0	
0	1	
1	0	
1	1	

(2 marks)

**8 (b)** A line-following robot has three sensors. It moves along a black line on a white background whilst the following conditions are met:

- the ultrasonic sensor U does not detect any obstacle
- either, but not both, of the infrared sensors L and R are on the black line.

Sensor U returns 1 if it detects an obstacle and 0 if the path is clear.

Sensors L and R each return 1 if they detect black and 0 if they detect white.

A logic circuit will process the input from the sensors and produce an output M.

M should be 1 if the robot is to move and 0 if the robot should stop.


**8 (b) (i)** Represent the output M as a Boolean expression.

M = .....


(3 marks)



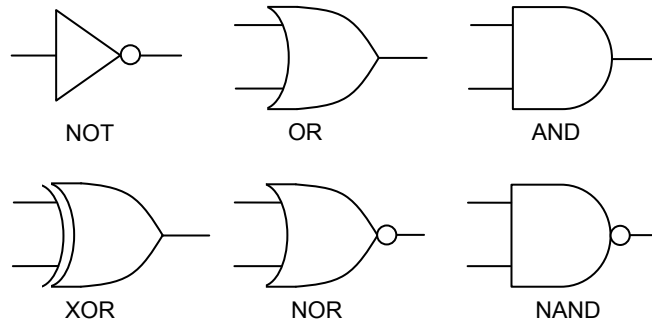8 (b) (ii) The following symbols are used to represent logic gates:



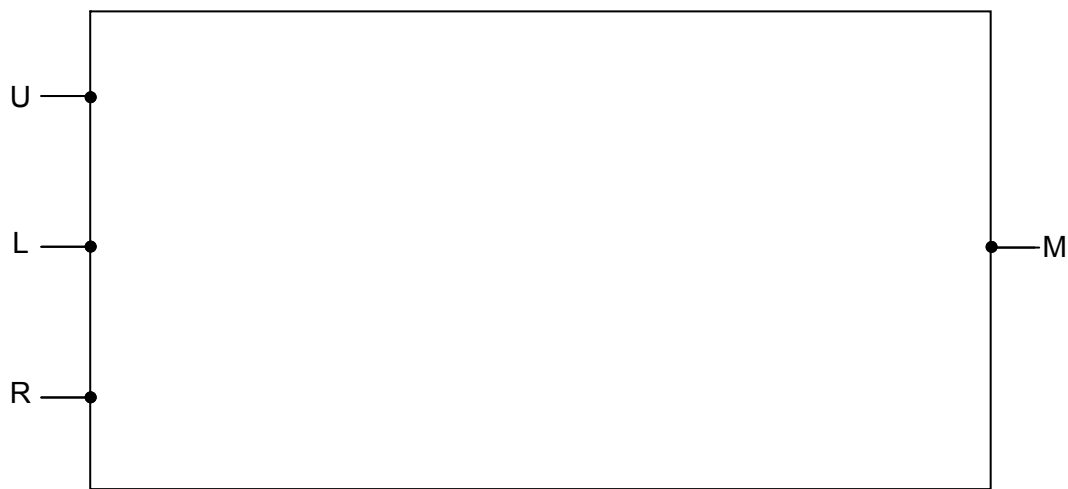Using a combination of any of the above logic gates draw a logic circuit for this system in the box below. You will **not** need to use all of the different types of logic gates.



(3 marks)

8 (c) Apply De Morgan's Law(s) to the following expression and simplify the result.

$$Q = \overline{\overline{A + (B \cdot A)}}$$

Show the stages of your working.

.....  
 .....  
 .....  
 .....

(2 marks)

Final answer .....

(1 mark)

